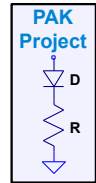


PAK Project – Course Material

PAK30x – Welcome. The W-function analytical approach

free for use under [Creative Commons 4 Attribution](https://creativecommons.org/licenses/by/4.0/). 22 Nov 2018 ver 0v1



Level 3 – How to solve multi-transistor circuits

PAK301 – Basic push-pull

PAK302 – Darlington push-pull

PAK303 – CFP push-pull


PAK304 – Current Feedback Amplifier

PAK305 – Spare

PAK306 – Faran-AB double displacement Class-AB+C

PAK307 – Double displacement Class-AB+C (Vdriven)

NEW PAK304 – CFP push-pull analysis as a CFP

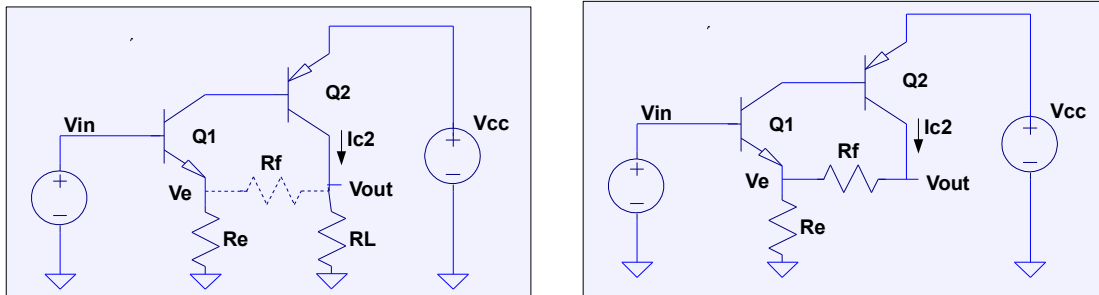

PAK304a. Complementary Feedback Pair (CFP) Open-Loop [L] and with Rf [R]

Q1 represents the CFA Diamond input stage. Q2 represents the CFA mirror and unity gain buffer with equivalent current gain $\beta_{2} \approx 10,000$. V_{in} drives Q1 with R_e degeneration. Q2 drives the output (R_L) plus R_f and R_e .

Open-Loop

Assume R_f feedback is disconnected and current flows to ground via R_L .

PAK 103 solves the Common Emitter amplifier with emitter degeneration R_e .

The Shockley equation gives the collector current as

$$I_c = I_s \left[e^{\left(\frac{V_{be}}{V_t} \right)} - 1 \right] \Rightarrow I_c = I_s \left[e^{\left(\frac{V_{in} - I_e \cdot R_e}{V_t} \right)} - 1 \right]$$

The solution for Q1 is

$$I_{c1_{ol}} = \frac{V_t}{R_{eq}} W \left[e^{\left(\frac{V_{in} - V_k}{V_t} \right)} \right] - I_{s1} \quad \text{where}$$

$$V_k = V_t \cdot \ln \left(\frac{V_t}{I_{s1} \cdot R_{eq}} \right) - I_{s1} \cdot R_{eq} \quad \text{and} \quad R_{eq} = R_e \cdot \left(\frac{1 + \beta_{a1}}{\beta_{a1}} \right)$$

where $W[\dots]$ is the W-function (a.k.a. Lambert's W-function), V_k is the knee voltage of about 0.6 volts where the transistor current reaches a typical current the mA range. R_{eq} is the emitter resistance referred to the collector side since the Schottky equation defines I_c and we want to solve for I_c and not I_e .

Now we know I_{c1} in terms of V_{in} we can calculate I_{c2} using $I_{c2} = \beta_{a2} \cdot I_{c1}$.

So Open-Loop solution for I_{c2} (output current) is

$$I_{c2} = \beta_{a2} \frac{V_t}{R_{eq}} W \left[e^{\left(\frac{V_{in} - V_k}{V_t} \right)} \right] - \beta_{a2} \cdot I_{s1}$$

The Open-Loop output voltage using Ohm's Law is $V_{out} = I_{c2} \cdot R_L$

Closed-Loop

The R_f feedback is connected and lets assume no current flows to ground via R_L .

The solution for Q_1 is now different to the Open-Loop equation because I_{c2} now flows through R_f . We can subtract an extra voltage $I_{c2} \cdot R_s$ from V_{in} by using Superposition

$$I_{c1} = \frac{V_t}{R_e} W \left[e^{\left(\frac{V_{in} - I_{c2} \cdot R_e - V_{k_1}}{V_t} \right)} \right] - I_{s_1} \quad \text{where } V_k, R_{eq} \text{ are still the same as before.}$$

Applying the W inverse to our new I_{c1} equation gives

$$I_{c1_{CL}} = \frac{V_t}{R_{eq_{CL}}} W \left[e^{\frac{V_{in} - V_{k_{CL}}}{V_t}} \right] - I_{s_1} \quad \text{where}$$

$$R_{eq_{CL}} = R_e \cdot (\text{Beta}2 + 1) \quad \text{and} \quad V_{k_{CL}} = V_t \cdot \ln \left(\frac{V_t}{I_{s_1} \cdot R_{eq_{CL}}} \right) - I_{s_1} \cdot R_{eq_{CL}}$$

Notice the R_{eq} value is multiplied by $\text{Beta}2$, effectively $\text{Beta}2$ times more degeneration for a given resistance. Also the V_k knee voltage is reduced, effectively Q_1 turns on 60mV/decade of $\text{Beta}2$ earlier (eg 120mV for a Beta of 100).

Using $I_{c1_{CL}}$ we calculate I_{c2} using $I_{c2} = \text{Beta}2 \cdot I_{c1}$.

So the Closed-Loop solution for I_{c2} (output current) is

$$I_{c2_{CL}} = \text{Beta}2 \frac{V_t}{R_{eq_{CL}}} W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right] - \text{Beta}2 \cdot I_{s_1} \quad \text{where } V_{k_{CL}} \text{ and } R_{eq_{CL}} \text{ are given above.}$$

The $\text{Beta}2$ term almost cancels with the R_{eq} term giving

$$I_{c2_{CL}} = \frac{V_t}{R_e} W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right] - \text{Beta}2 \cdot I_{s_1}$$

The Closed-Loop output voltage using Superposition is

$$V_{out} = I_{c2} \left(R_f + R_e \frac{\text{Beta}2 + 1}{\text{Beta}2} \right)$$

where $B2/(B2+1)$ is from some I_{c1} flowing through R_e as I_{e1} .

In terms of V_{in} Closed-Loop and with no load we get

$$V_{out} = \left(R_f + R_e \frac{\text{Beta}2 + 1}{\text{Beta}2} \right) \frac{V_t}{R_e} W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right] - \text{Beta}2 \cdot I_{s_1}$$

Simplifying and neglecting the $\text{Beta}2 \cdot I_{s1}$ term and with $B2$ large gives

$$V_{out} \simeq \left(\frac{R_f}{R_e} + 1 \cdot \frac{\text{Beta}2 + 1}{\text{Beta}2} \right) V_t \cdot W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right]$$

With $\text{Beta}2$ large the I_{c1} component through I_e is negligible, then

$$V_{out} \simeq \left(\frac{R_f}{R_e} + 1 \right) V_t \cdot W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right]$$

The incremental gain dV_{out}/dV_{in} is found by differentiation of the W -function (PAK114) gives

$$\frac{\partial V_{out}}{\partial V_{in}} \simeq \left(\frac{R_f}{R_e} + 1 \right) \frac{W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right]}{1 + W \left[e^{\left(\frac{V_{in} - V_{k_{CL}}}{V_t} \right)} \right]}$$

The ratio $W[\dots]/(1+W[\dots])$ reaches 91% of the ultimate Closed-Loop gain of $(R_f+R_e)/R_e$ when

V_{in} (the dc bias) is 60mV more than $V_{k_{CL}}$.

Notice this is the same ultimate voltage gain for a non-inverting Voltage Feedback amplifier when the feedback loop gain becomes very large.

The ratio $1/(1+W[...])$ represents the feedback "depth" or the feedback loop gain in dB is $20 \cdot \text{Log}(1+W[...])$. so for say 40dB feedback depth $W[...]\approx 100$ which occurs V_{in} (the dc bias) is $2 \times 60\text{mV}$ higher than $V_{k_{CL}}$, or in terms of $I_{c2} \approx 100 \cdot V_t / R_e$ which gives $V_{re} = I_{c2} \cdot R_e \approx 100 \cdot V_t$ and $100 \cdot V_t$ is 2.6 volts at 300K or 27C. If we chose R_e of say 100 ohms then I_{c2} would be 2.6/100 amps or 26mA for 40dB of feedback loop gain.

Compare this to the R_e method where $g_m \approx V_t / I_c$ or 26mA/V per mA, giving a g_m of 625mA/V at 26mA. The degenerated g_m with 100 ohms is 10mA/V so the internal g_m is about 62 times higher with about 36dB of loop gain which is close to the 40dB above.

What advantage does the W -solution offer compared to the commonly used small signal $1/r_E = g_m \approx V_t / I_c$ or 26 $\Omega \cdot \text{mA}$ method? [ref: Blundell A J, 'New approach to transistor circuit analysis', WW June 1971 p287-292, Pt 2 July 1971 <https://www.americanradiohistory.com/Archive-Wireless-World/70s/Wireless-World-1971-06.pdf> → p73 of PDF]

In a practical single ended amplifier will be a DC bias plus an AC component. The r_E method requires the DC operating point, then find all the small signal g_m 's and solve the linearised equations [ref Jarmo Lähdevaara <http://www.guitarscience.net/papers/feedback.pdf>]

First, using the W -approach we get a large signal solution for I_{C2} for Closed-Loop feedback and this gives a large signal equation for V_{out} in terms of the large signal V_{in} . Once I_{C2} is known all the other voltages and currents can be found by back substitution. Also the incremental gain at the DC bias point can be known in terms of all the circuit components. In small signal analysis you cannot calculate the DC bias point directly – you have to use approximations, or a graphical method, or use a simulator, or better from a bench test.

Also the 2nd and 3rd harmonic distortion can be calculated in terms of all the circuit components and in terms of the DC bias point – all are variables in the HD2 and HD3 equations so the designer has full information about the circuit currents, voltages, gains and low order distortion components including the thermal effects. PAK117 covers HD2 and HD3 calculation for the CE amplifier with shunt feedback and emitter degeneration.

More sophisticated secondary effects can be added including hitting V_{ce} saturation limits (PAK208), Beta variation with current (PAK208) and the Early effect (PAK209).

High frequency effects cannot be analysed (yet) using W -solutions – HF effects still requires transient simulations using a simulator. Stability analysis using W -analysis using numerical integration offers advantages over the conventional approach [ref: Ulsoy 2009 <https://pdfs.semanticscholar.org/5689/dc4c419177a36f2ab1b3726dc6a672b87448.pdf>]

In summary, using the W -approach we can have full understanding of how the circuit operates in Open-Loop and Closed-Loop for low frequency signals. With large signal equations we can optimise anything using partial differentiation for maxima/minima's including nulling temperature effects minimising nonlinearity and minimising distortion components.