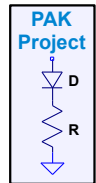


PAK Project – Course Material

PAK209 – BJT modelling for Early effect – excerpt

free for use under [Creative Commons 4 Attribution](https://creativecommons.org/licenses/by/4.0/) 17 Jan 2019 ver 0v5



New BJT modelling for Early effect

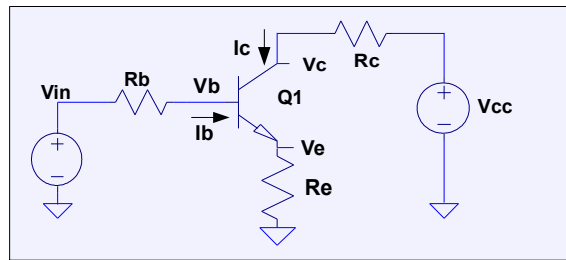


Fig209a.(Fig103a copy) **Basic CE with emitter degeneration**

Thought was given to how to get an exact solution for I_c using the W-approach. The problem is in the SPICE Gummel Poon (GP) model the Early effect uses

$$I_c = I_{c0} (1 + V_{ce}/V_A)$$

where I_{c0} is from the Shockley equation and $V_{ce} = V_{cc} - I_c \cdot R_{TOT}$ which gives

$$I_c / (1 + (V_{cc} - I_c \cdot R_{TOT}) / V_A) = I_{c0}$$

This gives an I_c term in the denominator which does not allow an exact W-solution.

Instead the original form for the Early effect as used in the improved VBIC [ref [BCTM98 text](#)])

$$I_c = I_{c0} / (1 - V_{ce}/V_E) \text{ giving}$$

$$I_c (1 - (V_{cc} - I_c \cdot R_{TOT}) / V_E) = I_{c0}$$

which requires a solution to $I_c (1 + b \cdot I_c) e^{k I_c} = e^{V_{in}/V_T}$. PAK113 allows an approximate solution (see below) with recursion to obtain whatever number of digit accuracy is desired. It turns out the V_E in the above equations needs to be twice the V_{EF} parameter in the LTspice VBIC (level=9) model and V_{EF} maps approximately equal to V_A (above) in the GP model.

Early tests on a TIP31A

A test on a TIP31A (100V 3A NPN) was done to fit to the alternative VBIC Early equation

$$I_c = I_{c0} / (1 - V_{ce}/V_E)$$

Fig.209b is a plot of $1/I_c$ versus V_{ce} . The V_{ce} intercept V_E is about 110V. For comparison the data was plotted to find the V_A intercept using the standard GP/EM equation and V_A is about 60V or close to half the alternative VBIC Early voltage V_E . Test voltages are V_{ce} of 8V and 32V at 100uA up to 13mA.

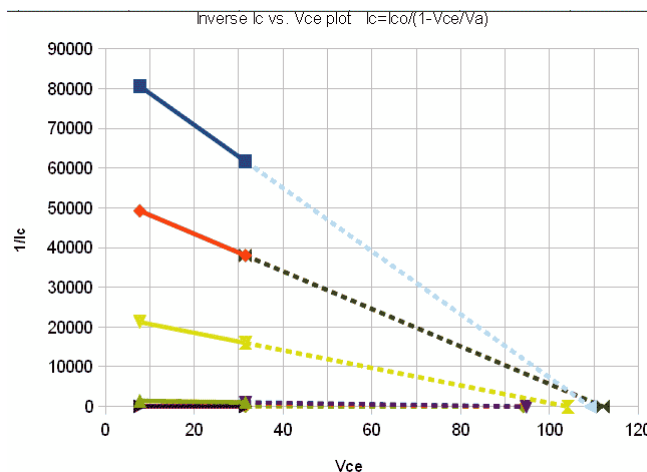


Fig.209b. TIP31A tests plot of 1/Ic versus Vce for the X-intercept V_A

The measured V_{ceo} (base open) breakdown voltage was 130V at 0.25mA. This suggests the alternative VBIC equation could be used to model both the Early effect and V_{ce} breakdown with one parameter (albeit only approximately for V_{ce_{max}} if a best fit is for V_E). Further tests are needed to check typical V_{ceo} breakdown voltages compared to the V_E parameter.

Figure 209c shows plots the currents and derivatives for the GP (standard SPICE) transistor with the Early effect and the VBIC Early effect formulation. The VBIC has some smoothing added seen in the derivative plot around clipping (this may be due to quasisaturation in the VBIC but I could not turn this rounding effect off) which is not modelled in my VBIC Early equation above and is therefore not seen in my Ealy effect solutions below.

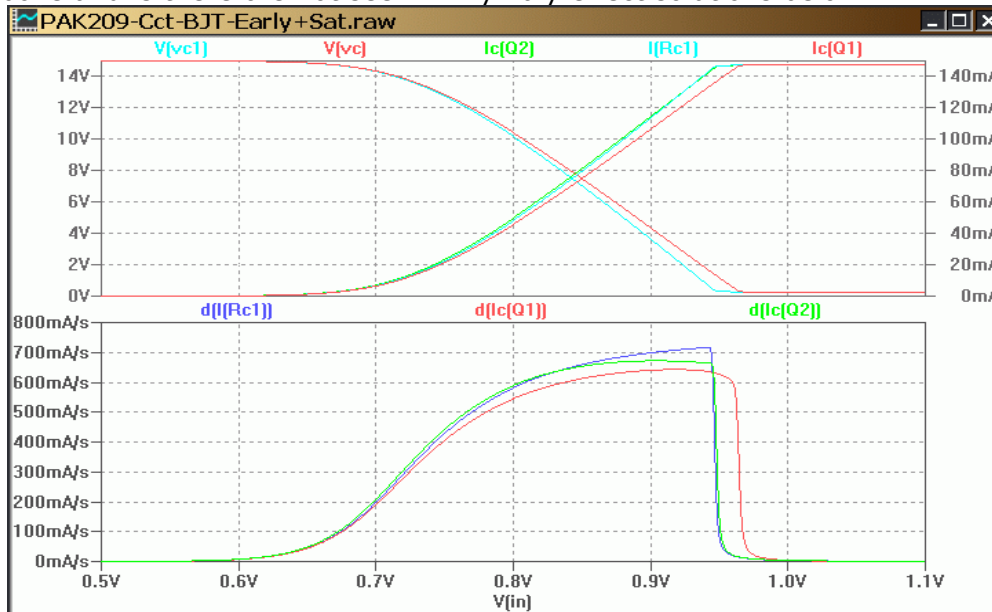


Figure 209c. GP Early effect (Q1) and the VBIC Early effect:

Plot values V_{AF}=V_E=20V, V_{cc}=15, I_s=10e-15, R_e=1, R_b=100, R_c=100, Beta= 100.

For these plots I have set V_{AF} to 20V and V_{cc} to 15V to see the difference clearly. The differences are sensitive to how close the peak V_{ce} gets to V_E in the VBIC formulation since V_E (as mentioned) is also the breakdown voltage (V_{ce_{max}}) and in my model equations using V_E (V_{eo} in the LTspice equations) 'breaks down' at 2*V_{EF} of the VBIC model or 40V the plot above.

New BJT modelling for Early effect excerpt below:

Using the improved VBIC [ref [BCTM98 text](#)] Early effect formulation:

$$I_c = \frac{I_{so}}{1 - \frac{V_{ce}}{V_E}} \left(e^{\frac{V_{be}}{V_t}} - 1 \right) \text{ where } V_E \text{ is the VBIC Early effect (different to EM/GP).}$$

Base $V_{be} = I_e \cdot R_e + \frac{I_c}{\beta} R_b$ where Beta depends on V_{ce}, $\beta = \frac{\beta_0}{1 - \frac{V_{ce}}{V_E}}$ where Beta₀ is 'BF'.

$$\Rightarrow V_{be} = I_e \cdot R_e + \frac{I_c}{\beta_0} R_b \left(1 - \frac{V_{ce}}{V_E} \right) \Rightarrow V_{be} = I_c \left(\frac{\beta_0 + 1}{\beta_0} \right) R_e + \frac{I_c}{\beta_0} R_b \left(1 - \frac{V_{ce}}{V_E} \right) = I_c \cdot R_{eq}$$

where $Req = \left(\frac{Beta + 1}{Beta}\right) Re + \frac{Rb}{Beta_0} \left(1 - \frac{Vce}{V_E}\right) = Re' + \frac{Rb}{Beta_0} \left(1 - \frac{Vce}{V_E}\right)$ where

$$Re' = \left(\frac{Beta + 1}{Beta}\right) Re \approx \left(\frac{Beta_0 + 1}{Beta_0}\right) Re$$

Substitute $Vbe = Vin - Ic \cdot Req$ gives $Ic = \frac{Is}{1 - \frac{Vce}{V_E}} \left(e^{\frac{Vin - Ic \cdot Req}{Vt}} - 1 \right)$

Substitute $Vce = Vcc - Ic(Rc + Re')$ gives $Ic = \frac{Is}{1 - \frac{Vcc - Ic \cdot (Rc + Re')}{V_E}} \left(e^{\frac{Vin - Ic \cdot Req}{Vt}} - 1 \right)$

Note: $Ic(Rc + Re')$ has Re' because Re' includes the Ib component.

The ' $Ic \cdot Req$ ' exponent has a variable Req due to $Beta(Vce)$. The Req term is expanded:

$$Req = Re' + \frac{Rb}{Beta_0} \left(1 - \frac{Vcc - Ic \cdot (Rc + Re')}{V_E}\right) = Re' + \frac{Rb}{Beta_0} \left(1 - \frac{Vcc}{V_E}\right) + \frac{Rb}{Beta_0} \frac{Rc + Re'}{V_E} Ic \text{ giving}$$

$$Req = Req_0(1 + m \cdot Ic) \text{ where } m = \frac{1}{Req_0} \frac{Rb}{Beta_0} \frac{Rc + Re'}{V_E} \text{ and } Req_0 = Re' + \frac{Rb}{Beta_0} \left(1 - \frac{Vcc}{V_E}\right)$$

Substitute Req and move the Is terms to LHS PAK200 series p3 of 7

$$Ic \left(1 - \frac{Vcc - Ic \cdot (Rc + Re')}{V_E}\right) + Is = Is \cdot e^{\frac{Vin - Ic \cdot Req_0(1 + m \cdot Ic)}{Vt}} \Rightarrow$$

$$Ic \left(\left(1 - \frac{Vcc}{V_E}\right) + \frac{(Rc + Re')}{V_E} Ic \right) + Is = Is \cdot e^{\frac{Vin - Req_0(1 + m \cdot Ic) \cdot Ic}{Vt}}$$

$$Ic \left(1 - \frac{Vcc}{V_E}\right) \left(1 + \frac{(Rc + Re') Ic}{V_E \left(1 - \frac{Vcc}{V_E}\right)}\right) + Is = Is \cdot e^{\frac{Vin - Req_0(1 + m \cdot Ic) \cdot Ic}{Vt}} \Rightarrow$$

$$Ic \left(1 - \frac{Vcc}{V_E}\right) (1 + n \cdot Ic) + Is = Is \cdot e^{\frac{Vin - Req_0(1 + m \cdot Ic) \cdot Ic}{Vt}} \text{ where } n = \frac{Rc + Re'}{V_E \left(1 - \frac{Vcc}{V_E}\right)}$$

giving $\left[Ic(1 + n \cdot Ic) + \frac{Is}{1 - \frac{Vcc}{V_E}} \right] e^{\frac{Req_0(1 + m \cdot Ic) \cdot Ic}{Vt}} = \frac{Is}{1 - \frac{Vcc}{V_E}} e^{\frac{Vin}{Vt}}$

It is not possible to solve this exactly for Ic since m and n are not *in general* equal ($m=n$ requires that $Re=0$). To get a solution we need a $(1+m \cdot Ic)$ term in the LHS mantissa which can be obtained by dividing both sides by $(1+n \cdot Ic)$ then multiplying by $(1+m \cdot Ic)$. This creates a ratio term $(1+m \cdot Ic)/(1+n \cdot Ic)$ on the RHS and this ratio is called a Switch function (Sw). Although an explicit solution cannot be obtained this way, we can use recursion to get whatever accuracy we need. We begin with an estimate Ic_{est} for the RHS ratio of m 's and n 's that use Ic .

Let $S_w = \frac{1+m \cdot I_c}{1+n \cdot I_c}$. Multiply both sides by $(Req_0/V_t)S_w$

$$\frac{Req_0}{V_t} \left(Sw \cdot Ic (1+n \cdot Ic) + \frac{Sw \cdot Is}{1 - \frac{V_{cc}}{V_E}} \right) \cdot e^{\frac{Req_0(1+m \cdot Ic) \cdot Ic}{V_t}} = \frac{Sw Is Req_0}{V_t \left(1 - \frac{V_{cc}}{V_E} \right)} e^{\frac{V_{in}}{V_t}} \Rightarrow$$

$$\frac{Req_0}{V_t} \left(Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)} \right) \cdot e^{\frac{Req_0 \cdot Ic(1+m \cdot Ic)}{V_t}} = \frac{Sw Is Req_0}{V_t \left(1 - \frac{V_{cc}}{V_E} \right)} e^{\frac{V_{in}}{V_t}}$$

Now add 'Is·Sw' to the LHS and RHS exponents

$$\frac{Req_0}{V_t} \left(Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)} \right) e^{\frac{Req_0}{V_t} \left(Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)} \right)} = \frac{Sw Is Req_0}{V_t \left(1 - \frac{V_{cc}}{V_E} \right)} e^{\left(\frac{V_{in} + \frac{Sw \cdot Is Req_0}{\left(1 - \frac{V_{cc}}{V_E} \right)}}{V_t} \right)}$$

Simplify using Vks (knee voltage defined below) ready for the inverse W-solution

$$\frac{Req_0}{V_t} \left(Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)} \right) \cdot e^{\frac{Req_0 \cdot Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)}}{V_t}} = e^{\left(\frac{V_{in} - V_{ks}}{V_t} \right)}$$

where $V_{ks} = V_t \ln \left(\frac{V_t \left(1 - \frac{V_{cc}}{V_E} \right)}{Sw \cdot Is \cdot Req_0} \right) - \frac{Sw \cdot Is Req_0}{\left(1 - \frac{V_{cc}}{V_E} \right)}$, or $V_{ks} = V_{k_0} - V_t \ln(Sw) - \frac{(1-Sw) \cdot Is Req_0}{\left(1 - \frac{V_{cc}}{V_E} \right)}$

where $V_{k_0} = V_t \ln \left(\frac{V_t \left(1 - \frac{V_{cc}}{V_E} \right)}{Is \cdot Req_0} \right) - \frac{Is Req_0}{\left(1 - \frac{V_{cc}}{V_E} \right)}$ is the constant part of Vks

The W-solution

$$\frac{Req_0}{V_t} \left(Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)} \right) = W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t} \right)} \right] \Rightarrow$$

$$Ic(1+m \cdot Ic) + \frac{Sw \cdot Is}{\left(1 - \frac{V_{cc}}{V_E} \right)} = \frac{V_t}{Req_0} W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t} \right)} \right] \Rightarrow$$

$$m \cdot I_c^2 + I_c + \frac{S_w \cdot I_s}{\left(1 - \frac{V_{cc}}{V_E}\right)} = \frac{V_t}{Req_0} W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t}\right)} \right] \text{ divide by } m \text{ (for } m \neq 0, \text{ i.e. } R_b \neq 0),$$

$$I_c^2 + \frac{1}{m} I_c + \frac{S_w \cdot I_s}{m \left(1 - \frac{V_{cc}}{V_E}\right)} = \frac{V_t}{m \cdot Req_0} W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t}\right)} \right] \text{ complete the square}$$

$$\left(I_c + \frac{1}{2m}\right)^2 = \frac{V_t}{m \cdot Req_0} W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t}\right)} \right] + \left(\frac{1}{2m}\right)^2 - \frac{S_w \cdot I_s}{m \left(1 - \frac{V_{cc}}{V_E}\right)}$$

Square root and solve for I_c for $m \neq 0$ (i.e. $R_b \neq 0$) is

$$I_c = \frac{-1}{2m} + \sqrt{\left(\frac{1}{2m}\right)^2 + \frac{V_t}{m \cdot Req_0} W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t}\right)} \right] - \frac{S_w \cdot I_s}{m \left(1 - \frac{V_{cc}}{V_E}\right)}}$$

where $m = \frac{1}{Req_0} \frac{R_b}{Beta_0} \frac{R_c + R_e}{V_E}$, $n = \frac{R_c + R_e'}{V_E \left(1 - \frac{V_{cc}}{V_E}\right)}$, $S_w = \frac{1 + m \cdot I_{c_{est}}}{1 + n \cdot I_{c_{est}}}$ and

$$V_{ks} = V_{k_0} - V_t \ln(S_w) - \frac{(1 - S_w) I_s Req_0}{\left(1 - \frac{V_{cc}}{V_E}\right)} \text{ where } V_{k_0} = V_t \ln \left(\frac{V_t \left(1 - \frac{V_{cc}}{V_E}\right)}{I_s \cdot Req_0} \right) - \frac{I_s Req_0}{\left(1 - \frac{V_{cc}}{V_E}\right)} \text{ and}$$

$$Req_0 = R_e' + \frac{R_b}{Beta_0} \left(1 - \frac{V_{cc}}{V_E}\right), \quad R_e' = \left(\frac{Beta + 1}{Beta}\right) \cdot R_e \approx \left(\frac{Beta_0 + 1}{Beta_0}\right) \cdot R_e$$

The approximation for $I_{c_{est}}$ in 'Sw' determines the accuracy of the first I_c solution.

A good first approximation for I_c is the solution with $R_b = 0$ (derivation below)

$$I_{c_{est}} = \frac{V_t}{Req_0} W \left[e^{\left(\frac{V_{in} - V_{ks}}{V_t}\right)} \right] - \frac{I_s}{\left(1 - \frac{V_{cc}}{V_E}\right)} \text{ where } V_{k_0} \text{ is given above.}$$

This gives the correct starting knee voltage but $I_{c_{sat}}$ at clip ($I_{c_{sat}} \approx V_{cc}/(R_c + R_e)$) is too large and this deviation is corrected by further iterations.

How many recursions do I need?

With the V_{k_0} starting point for $I_{c_{est}}$ above the error with the *first* quadratic solution above for I_c was below $\sim 1\%$ when $R_b \approx Beta \cdot R_e$. So one calculation (other than the $I_{c_{est}}$ above) is OK for general analytic manipulations. I have chosen to use two recursions in general. But when R_e is small (< 0.1 ohm for a 100mA small-signal BJT) and if R_b is also small ($R_b < Beta \cdot R_e$) then a third recursion gets less than 1% error (but convergence is very slow in this situation). In LTspice the third recursion can be skipped using a conditional statement

If (U (Beta * Re - Rb) , 2nd, 1st).

Error can be checked when $V_{ce}=0$ which is when $I_{c_{sat}} = \frac{V_{cc}}{R_c + R_{e'}}$. With $V_{ce}=0$ $\beta = \beta_0$ and using the original Shockley equation $V_{in_{sat}} = I_{c_{sat}} \cdot R_e \left(\frac{\beta_0 + 1}{\beta_0} \right) + V_t \ln \left(\frac{I_{c_{sat}}}{I_s} + 1 \right)$.

Then use $V_{in_{sat}}$ to calculate I_c with Ratio=1. Then calculate the error $\alpha = \frac{I_c - I_{c_{sat}}}{I_{c_{sat}}}$ for the first iteration. The second iteration error allows the rate of convergence can be estimated (second error over the first error) for how many recursions are needed to get to your required accuracy. It depends on R_e, R_b, V_{cc} and V_A values, so a .param calculation can determine the number of recursions before the .trans V_{in} sweep. LTspice default Reltol is 0.001 (0.1%). Note the approximation $R_{e'} = R_e \left(\frac{\beta_0 + 1}{\beta_0} \right)$ where β_0 is used in place of the variable $\beta(V_{ce})$ may limit the ultimate accuracy unless a correction function is used to account for this. Further work is needed to improve this limit to the ultimate accuracy.

Figure 209d shows the I_c and V_c plots for a Common Emitter amplifier of **Fig.209a** above with $R_c=100$ ohms $\beta=100$, $V_E=20V$, $V_{cc}=15V$ and R_b and R_e are stepped over a wide range. This is a very pleasing solution. All plots are better than 0.1% with two recursions, the exception is $R_b=R_e=0.1$ with $\sim 1\%$ error with 2 recursions.

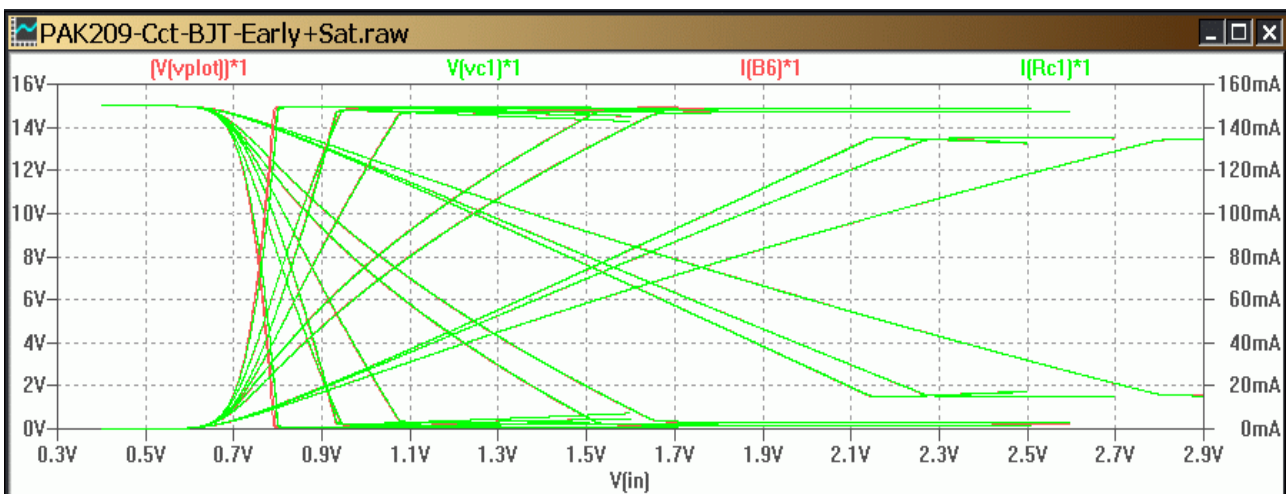


Fig. 209d. W-equations with Early and Saturation using two recursions. Step R_b 0.1 1 100 500, R_e 0.1 1 10, $I_s=1e-14$ $\beta=100$, $V_E=20$ $V_{cc}=15$ $R_c=100$.

Special case: $R_b=0$

If $R_b=0$ we get a divide by zero, so for $R_b=0$ $Req_0 = R_{e'}$, so $m=0$ giving $S_w = \frac{1}{1 + n \cdot I_c}$

Use the alternative W-solution below: Multiply both sides by $(R_{e'}/V_t)S_w$

$$\frac{Req_0}{V_t} \left(S_w \cdot I_c (1 + n \cdot I_c) + \frac{S_w \cdot I_s}{1 - \frac{V_{cc}}{V_E}} \right) \cdot e^{\frac{Req_0 I_c}{V_t}} = \frac{S_w I_s R_{e'}}{V_t \left(1 - \frac{V_{cc}}{V_E} \right)} e^{\frac{V_{in}}{V_t}} \Rightarrow$$

$$\frac{Req_0}{Vt} \left(Ic + \frac{Sw \cdot Is}{\left(1 - \frac{Vcc}{V_E}\right)} \right) e^{\frac{Req_0 Ic}{Vt}} = \frac{Sw Is Req_0}{Vt \left(1 - \frac{Vcc}{V_E}\right)} e^{\left(\frac{Vin + \frac{Sw \cdot Is Req_0}{\left(1 - \frac{Vcc}{V_E}\right)}}{Vt} \right)} \Rightarrow$$

$$\frac{Req_0}{Vt} \left(Ic + \frac{Sw \cdot Is}{\left(1 - \frac{Vcc}{V_E}\right)} \right) = W \left[e^{\left(\frac{Vin - Vks}{Vt} \right)} \right] \Rightarrow$$

$$Ic = \frac{Vt}{Req_0} W \left[e^{\left(\frac{Vin - Vks}{Vt} \right)} \right] - \frac{Sw \cdot Is}{\left(1 - \frac{Vcc}{V_E}\right)} \text{ where}$$

$$Sw = \frac{1}{1 + n \cdot Ic_{est}}, \quad n = \frac{Rc + Re'}{V_E \left(1 - \frac{Vcc}{V_E}\right)}, \quad Vks = Vk_0 - Vt \ln(Sw) - \frac{(1 - Sw) Is Req_0}{\left(1 - \frac{Vcc}{V_E}\right)} \text{ where}$$

$$Vk_0 = Vt \ln \left(\frac{Vt \left(1 - \frac{Vcc}{V_E}\right)}{Is \cdot Req_0} \right) - \frac{Is Req_0}{\left(1 - \frac{Vcc}{V_E}\right)}, \quad Req_0 = Re' + \frac{Rb}{Beta_0} \left(1 - \frac{Vcc}{V_E}\right), \text{ and}$$

$$Re' = \left(\frac{Beta + 1}{Beta} \right) \cdot Re \approx \left(\frac{Beta_0 + 1}{Beta_0} \right) Re$$

Note: When Rb=0 the same equations can be used $Sw = \frac{1 + m \cdot Ic_{est}}{1 + n \cdot Ic_{est}}$ (since m=0) and Vks

doesn't mind that Rb is 0; the only difference is the main equation for Ic which avoids the divide by zero (m=0). Typical LTspice numerical precision allows Rb to nano-ohms with an Re in the 1 ohm range (small-signal BJT) before needing to consider using the alternative equation for Rb=0.